

## Lab 9 - BJT DC Biasing

Ty Davis

ECE 3110

November 20, 2024

---

### Introduction

In this lab we are analyzing the DC operating points of an NPN-type BJT. There are three modes of operation for a BJT, namely *active*, *saturation*, and *cutoff*. We are going to analyze the BJT in both the *active* and *saturation* regions of operation.

Fig. 1 shows our circuit. For each mode of operation we will select different resistor values in order to bias the circuit.

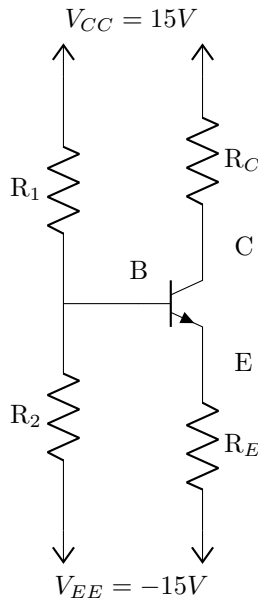


Figure 1: The circuit we use in the lab.

### Analysis

#### Active Mode Operation

For active mode operation we are going to design the circuit such that  $I_C = 1 \text{ mA}$ ,  $V_B = 0 \text{ V}$ , and  $V_C = 5 \text{ V}$ .

We can quickly find  $I_B$  because we know that  $\beta$  from the data sheet is  $\beta = 161.205$ . This means that  $I_B = I_C / \beta = 6.203 \text{ }\mu\text{A}$ . Knowing that  $I_E = I_C + I_B$ , we get  $I_E = 1.006203 \text{ mA}$ .

With these values we can find  $R_C = \frac{15-5}{1 \text{ mA}} = 10 \text{ k}\Omega$ . Using the constant drop model, we can assume that  $V_E = V_B - 0.7 \text{ V} = -0.7 \text{ V}$ . This leads us to  $R_E = \frac{-0.7 - (-15)}{1.006203 \text{ mA}} = 14.371 \text{ k}\Omega$ .

For the remaining two resistors, the function is not fully specified, but we know that  $V_B = 0 \text{ V}$ , and the current through  $R_1$  is equal to the current through  $R_2$  and the current  $I_B$ . As such, we can do some brief nodal analysis to find:

$$\frac{V_{CC} - 0}{R_1} + \frac{0 - V_{EE}}{R_2} + I_B = 0$$

Rearranging this to solve for  $R_1$  in terms of  $R_2$  we find this equation:

$$R_1 = V_{CC} \cdot \left( \frac{1}{-I_B - V_{EE}/R_2} \right)$$

That expression allowed us to choose some  $R_2$  and determine a necessary  $R_1$ . We chose the value  $R_2 = 100 \text{ k}\Omega$ , and the corresponding  $R_1$  is found to be  $R_1 = 96.028 \text{ k}\Omega$ .

## Saturation Mode Operation

The Saturation Mode operation is even more straightforward. We are going to design the circuit such that  $I_C = 1 \text{ mA}$ ,  $I_E = 0.2 \text{ mA}$ ,  $V_C = 2 \text{ V}$ , and  $V_{CE} = 0.2 \text{ V}$ .

Knowing  $I_C$  and  $I_B$  means that we can find  $I_E = 200 \text{ }\mu\text{A}$ . Also, we find that  $V_E = 1.8 \text{ V}$  because  $V_{CE} = 0.2 \text{ V}$ .

With values for  $V_C$  and  $V_E$  we can find that  $R_C = 13 \text{ k}\Omega$  and  $R_E = 14 \text{ k}\Omega$ .

The same method for calculating  $R_1$  and  $R_2$  applies in this circuit as well, so we can select  $R_2 = 100 \text{ k}\Omega$  and find that  $R_1 = 33.333 \text{ k}\Omega$ .

The  $\beta_{\text{forced}}$  that we found is  $\frac{1 \text{ mA}}{200 \text{ }\mu\text{A}} = 5$ .

## Simulation Results

Building the circuit in Multisim we recorded the following values:

	Active Mode	Saturation Mode
$V_C$	5.12 V	1.92 V
$V_B$	-40.0 mV	2.54 V
$V_E$	-0.704 V	1.86 V
$V_{BE}$	0.66 V	0.68 V
$V_{CE}$	5.82 V	0.08 V
$I_C$	0.988 mA	1.01 mA
$I_B$	7.02 $\mu\text{A}$	198.68 $\mu\text{A}$
$I_E$	0.995 mA	1.20 mA

Table 1: Simulation results.

## Measurement Results

Building the circuit we found that the our analysis and simulation in both active mode and saturation mode operation were very close to the actual performance of the device. Look at Tables 3 and 4 to see the resistor values that we used.

The  $\beta_{\text{forced}}$  that we calculated is  $\frac{1.012 \text{ mA}}{205.7 \text{ }\mu\text{A}} = 4.921$ .

	Active Mode	Saturation Mode
$V_C$	5.06 V	1.918 V
$V_B$	-3.0 mV	2.546 V
$V_E$	-0.661 V	1.873 V
$V_{BE}$	0.658 V	0.673 V
$V_{CE}$	5.721 V	0.045 V
$I_C$	1.00638 mA	1.01215 mA
$I_B$	5.12 $\mu$ A	205.68 $\mu$ A
$I_E$	1.0115 mA	1.21783 mA

Table 2: Measurement results.

Calculated Resistor	Equivalent Resistor	Measured Resistor	
10 k $\Omega$	10 k $\Omega$	9.877 k $\Omega$	$R_C$
14.371 k $\Omega$	14.347 k $\Omega$	14.176 k $\Omega$	$R_E$
	15 k $\Omega$	14.82 k $\Omega$	
	330 k $\Omega$	325.38 k $\Omega$	
96.028 k $\Omega$	96.2 k $\Omega$	95.542 k $\Omega$	$R_1$
	47 k $\Omega$	46.689 k $\Omega$	
	47 k $\Omega$	46.679 k $\Omega$	
	2.2 k $\Omega$	2.173 k $\Omega$	
100 k $\Omega$	100 k $\Omega$	98.75 k $\Omega$	$R_2$

Table 3: Active Mode Resistors.

Calculated Resistor	Equivalent Resistor	Measured Resistor	
13 k $\Omega$	13.043 k $\Omega$	12.925 k $\Omega$	$R_C$
	15 k $\Omega$	14.86 k $\Omega$	
	100 k $\Omega$	99.35 k $\Omega$	
14 k $\Omega$	14.042 k $\Omega$	13.855 k $\Omega$	$R_E$
	15 k $\Omega$	14.82 k $\Omega$	
	220 k $\Omega$	217.68 k $\Omega$	
96.028 k $\Omega$	96.2 k $\Omega$	95.542 k $\Omega$	$R_1$
	47 k $\Omega$	46.689 k $\Omega$	
	47 k $\Omega$	46.679 k $\Omega$	
	2.2 k $\Omega$	2.173 k $\Omega$	
100 k $\Omega$	100 k $\Omega$	98.75 k $\Omega$	$R_2$

Table 4: Active Mode Resistors.