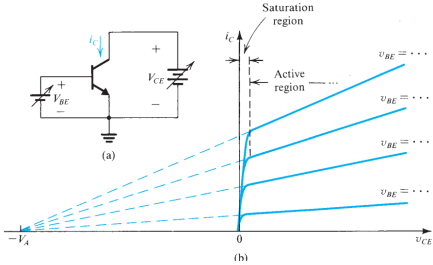


Chapter 6 - BJTs You need to go to page 357 in the text and find a bunch of the good expressions relating  $I_E$ ,  $I_B$  and  $I_C$ .  $I_S$  is known as Saturation Current We need to consider:  
 Base current  $I_B$   
 Collector current  $I_C$  and  
 Collector-emitter Voltage  $V_{CE}$

$$i_C = I_s e^{v_{BE}/V_T}$$



Considering the Early voltage


$$i_C = I_s e^{v_{BE}/V_T} \left( 1 + \frac{v_{CE}}{V_A} \right)$$

$$r_o = \left[ \frac{\delta i_c}{\delta v_{CE}} \Big|_{v_{BE}=\text{constant}} \right]^{-1}$$

$$r_o = \frac{V_A + V_{CE}}{I_C}$$

$$r_o = \frac{V_A}{I'_C}$$
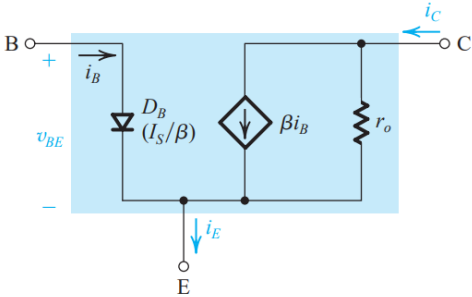
$$\text{Where } I'_C = I_s e^{V_{BE}/V_T}$$



$$R_{CE\text{SAT}} \equiv \frac{\delta v_{CE}}{\delta i_C} \Big|_{i_B=I_B | i_C=I_{C\text{SAT}}}$$

$$\frac{I_C}{I_B} = \text{transistor } \beta$$