

Graphical solution for voltage and current through diode.

