

Lab 7 Report

Ty Davis

November 6, 2023

1 Introduction

In this lab our task is to study the performance of an NMOS "Source Follower" or common-drain amplifier. We will first perform an analysis of the DC component of the circuit, then we will analyze its performance with small signals.

2 DC Analysis